
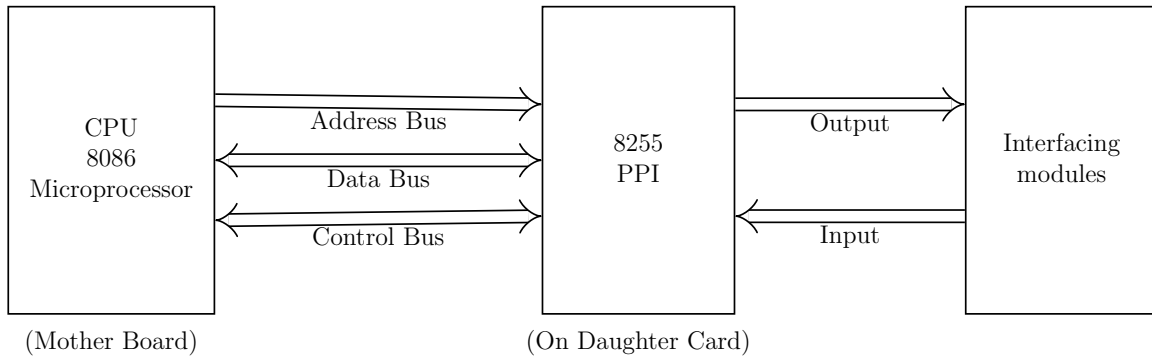


A Block Diagram of Interfacing Devices

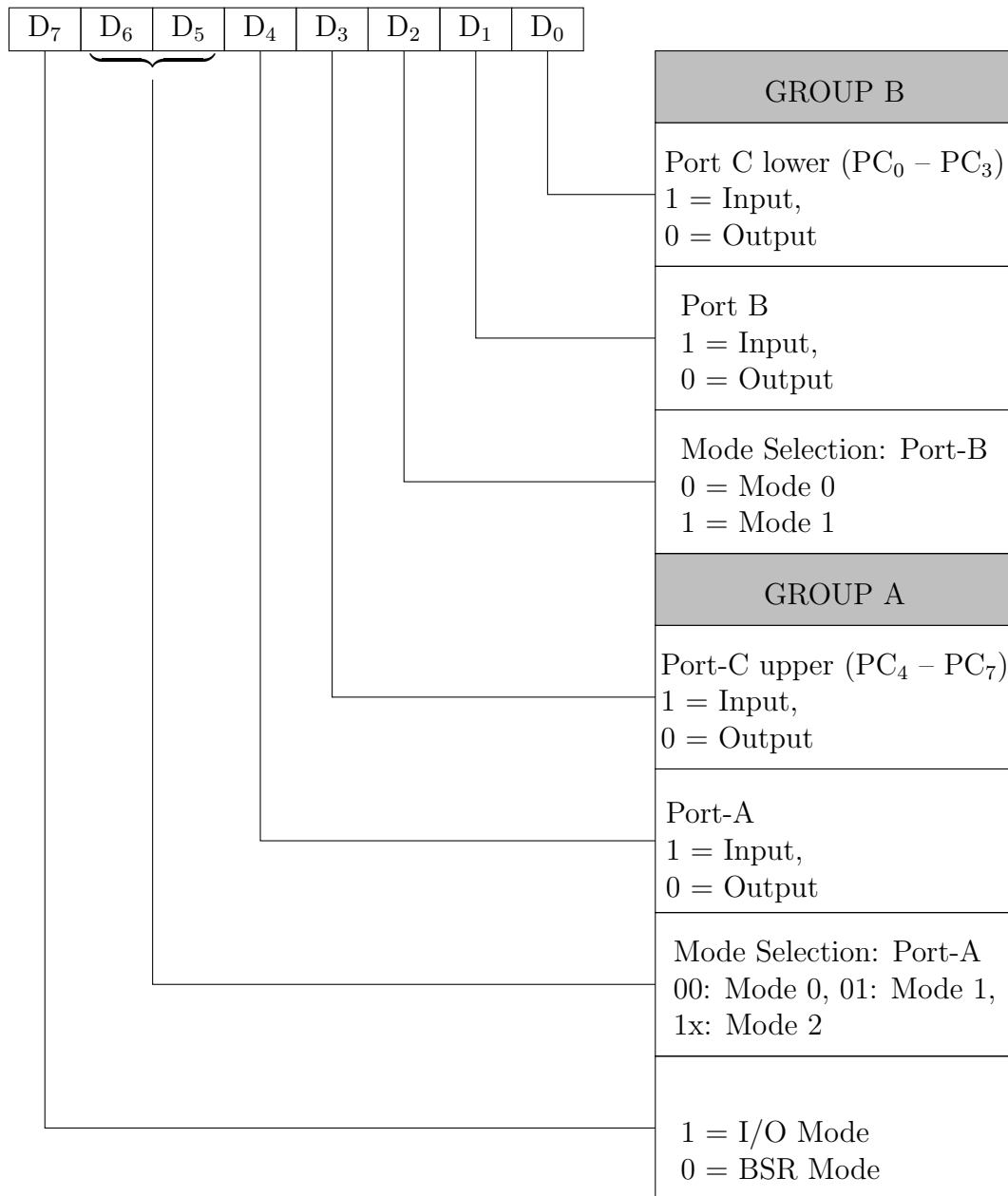
A.1 The general block diagram of Interfacing through 8255 PPI





A.2 The control word format of 8255 PPI



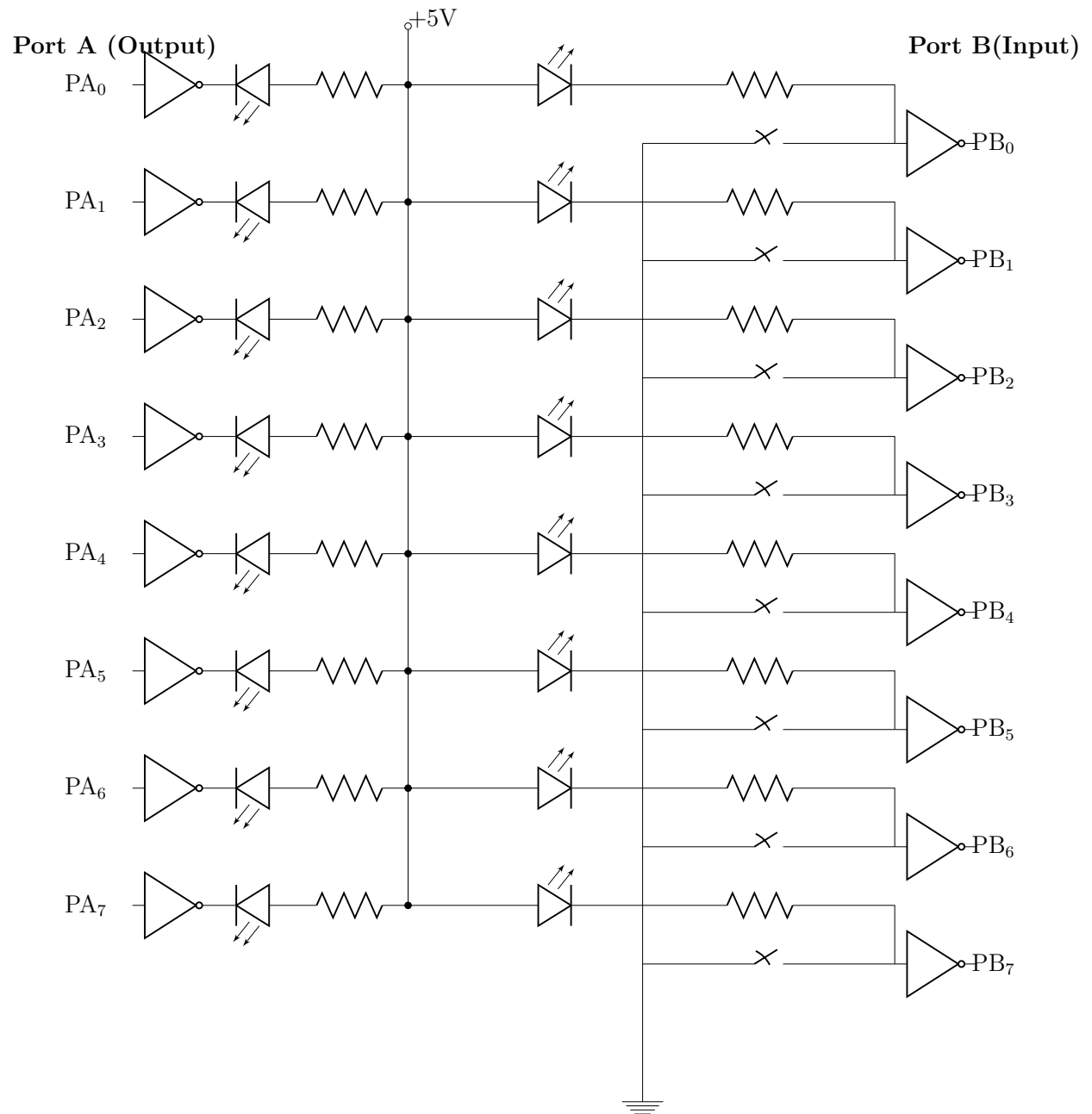
A.3 The circuit diagram of Logic Controller



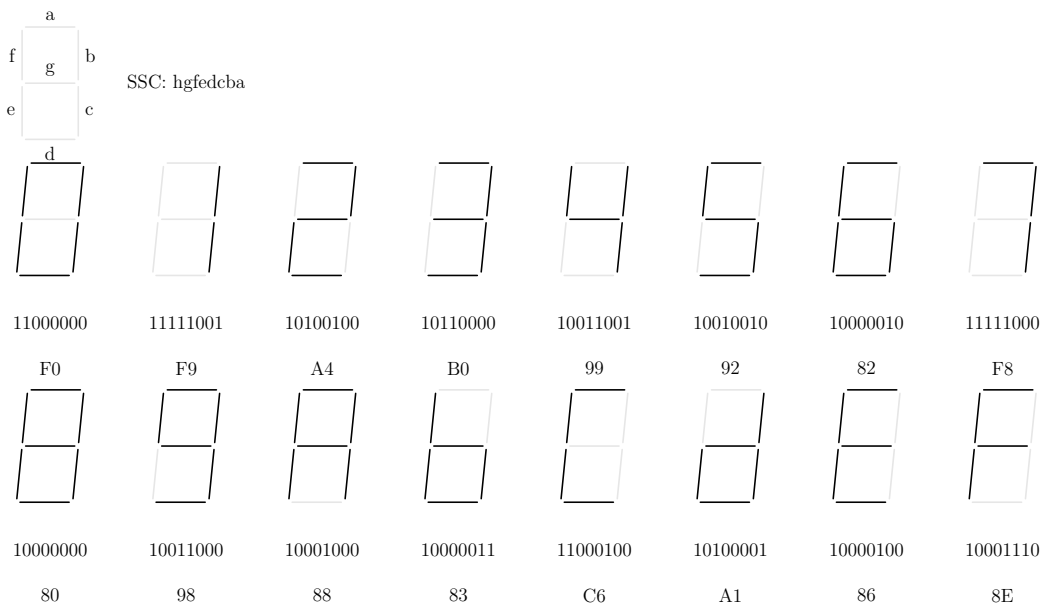
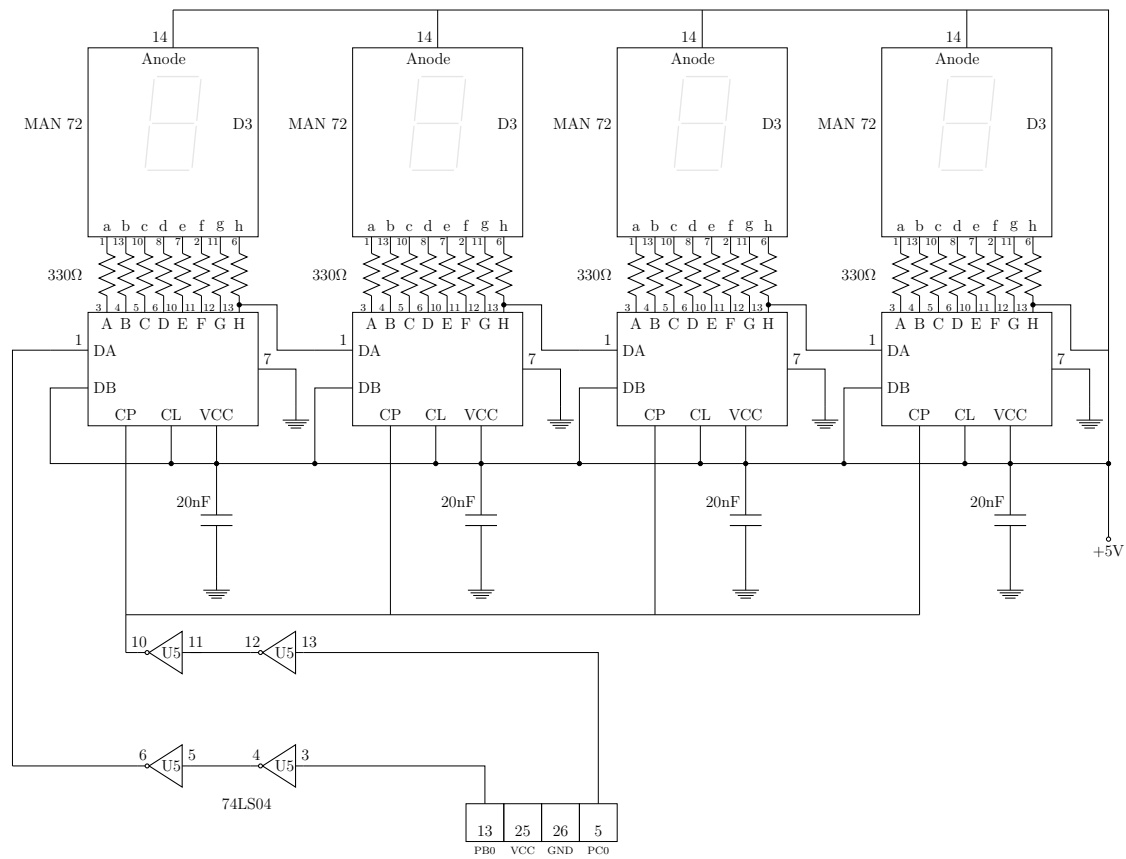
A.4 The circuit diagram of Display Interface




A.5 Keyboard Interface

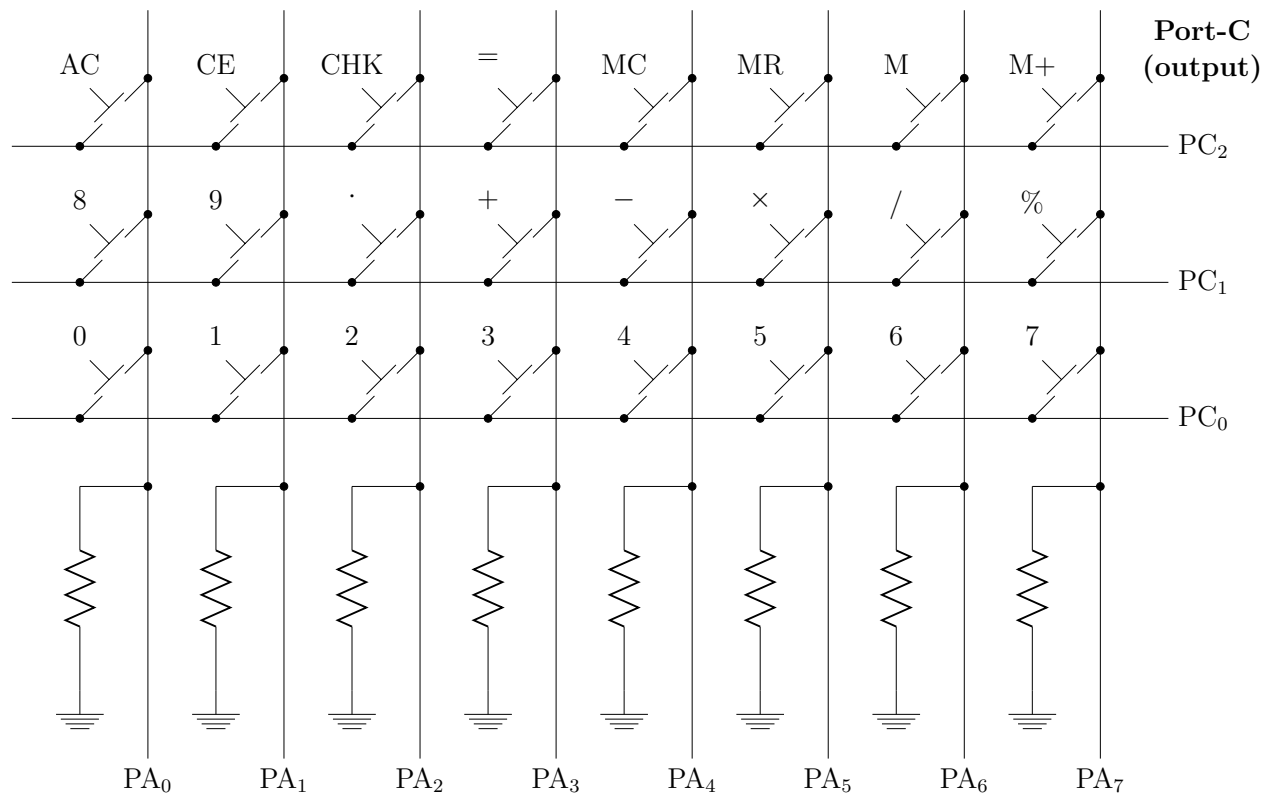


A.6 The circuit diagram of DAC Interface

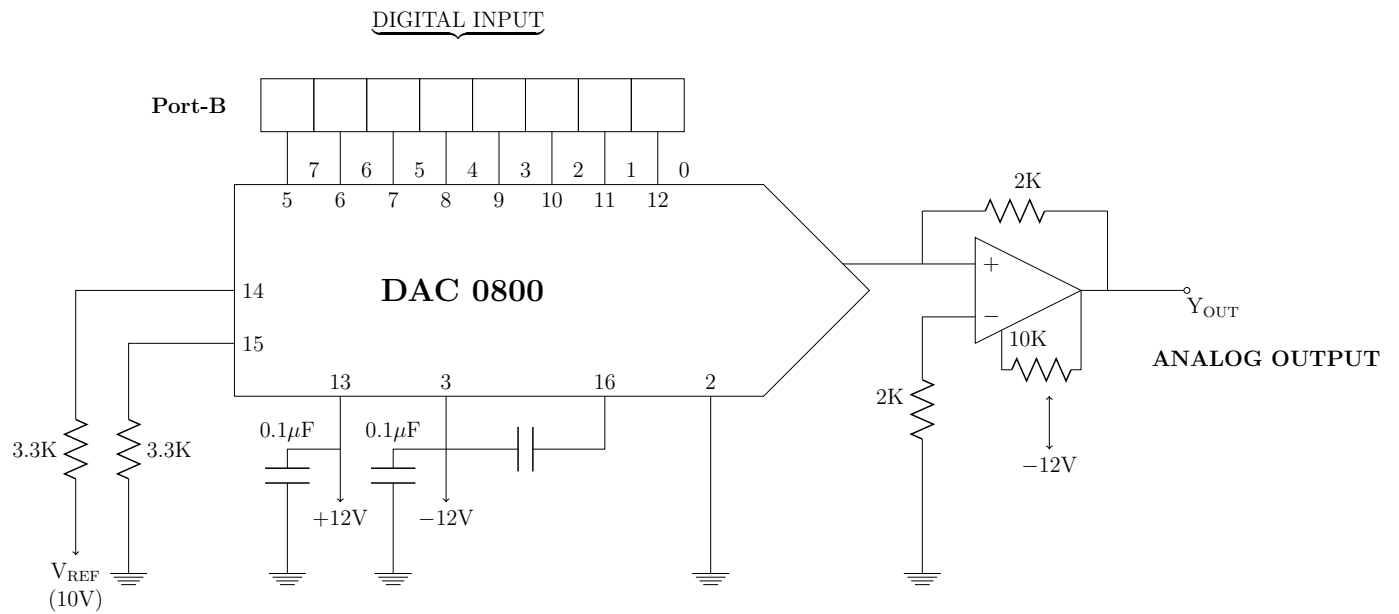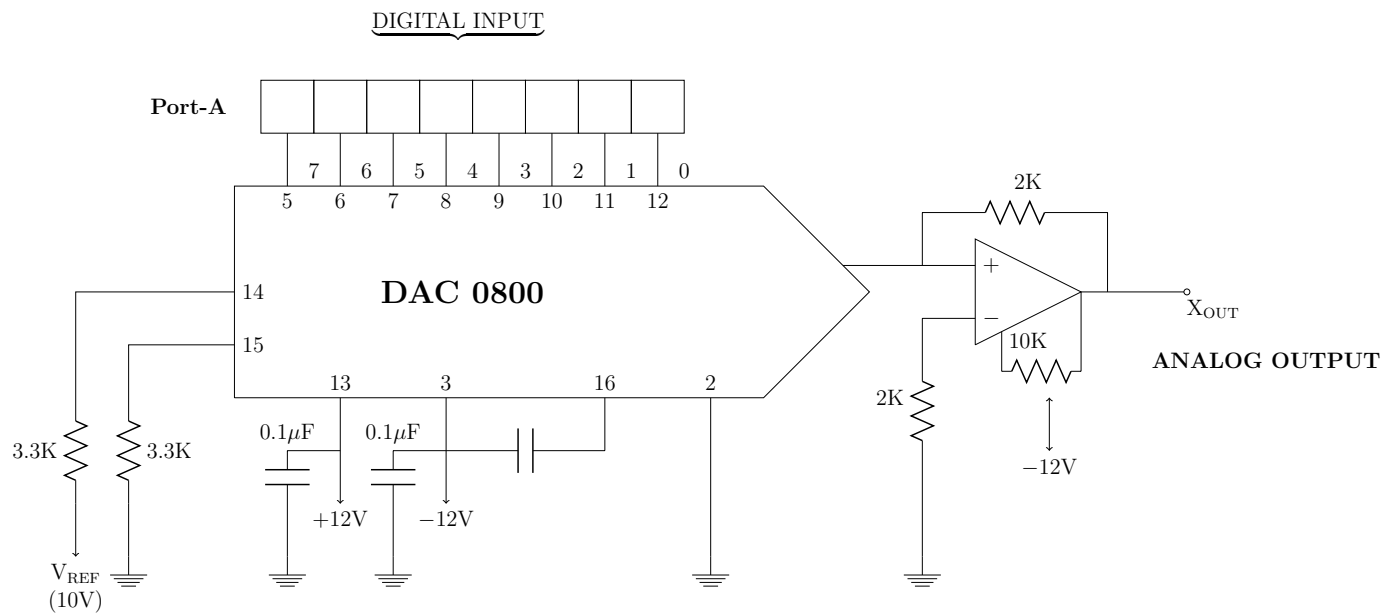


A.7 Elevator Interface

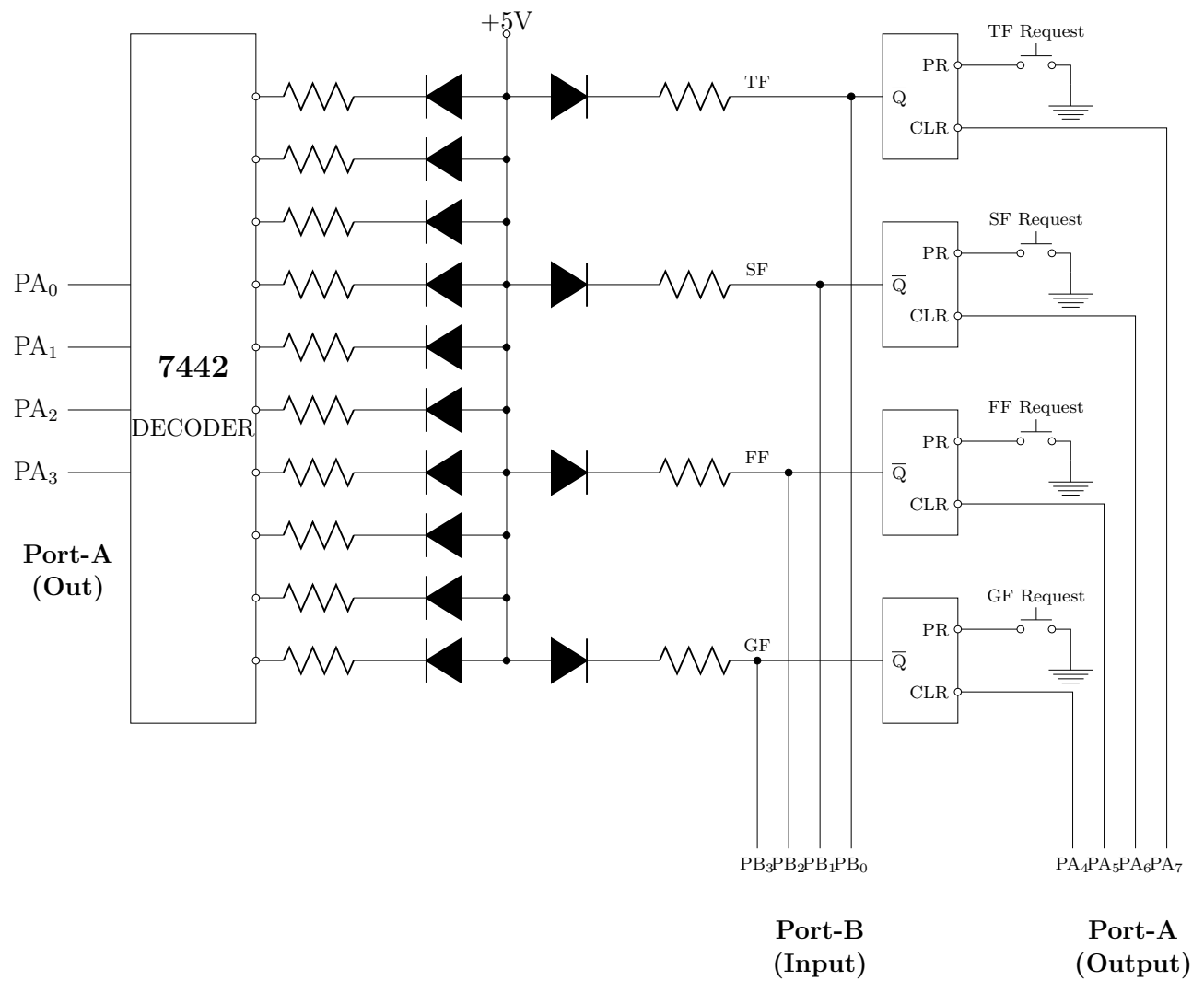

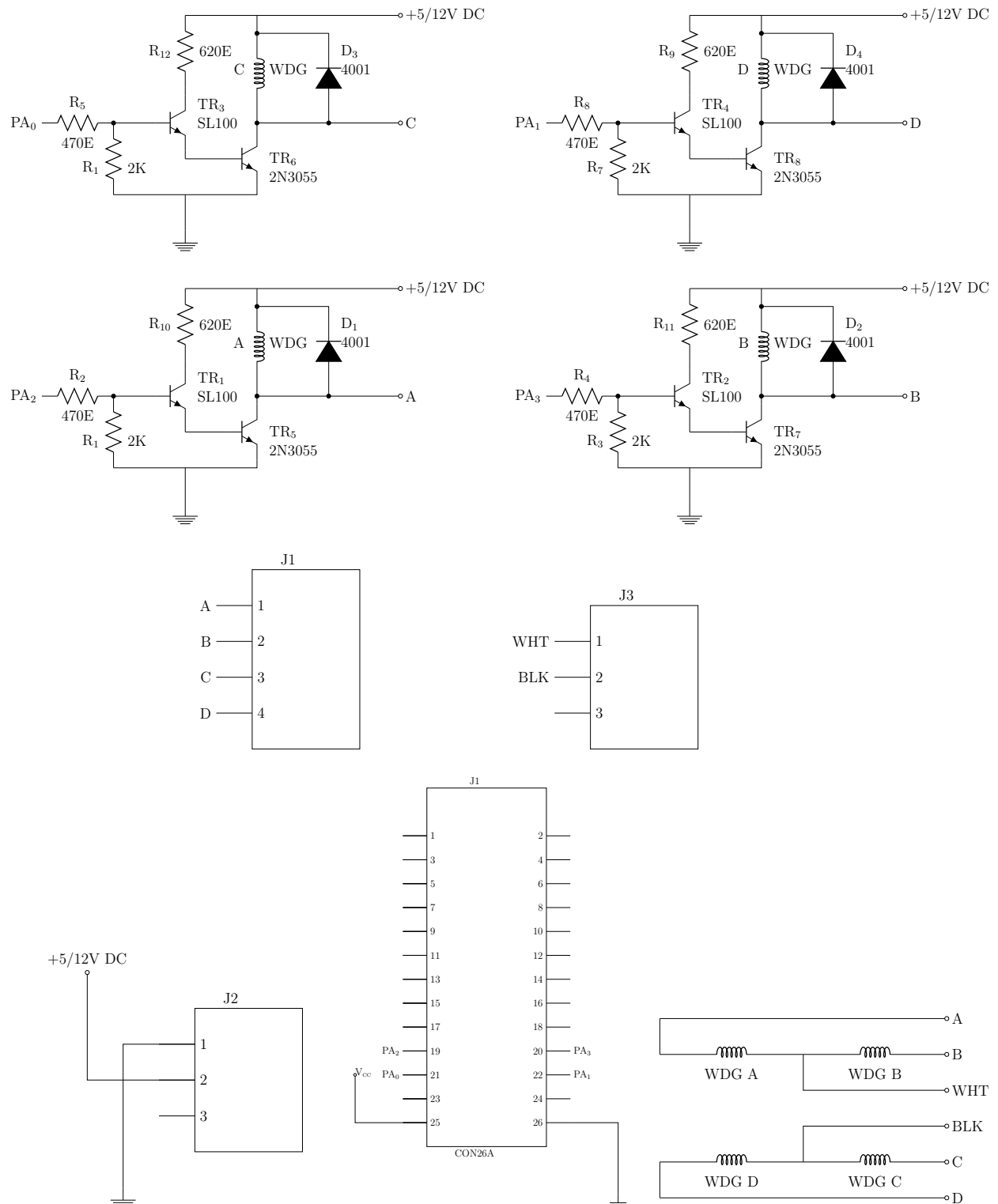A.8 The circuit diagram of Stepper Motor Driver



A.9 Control Word Format

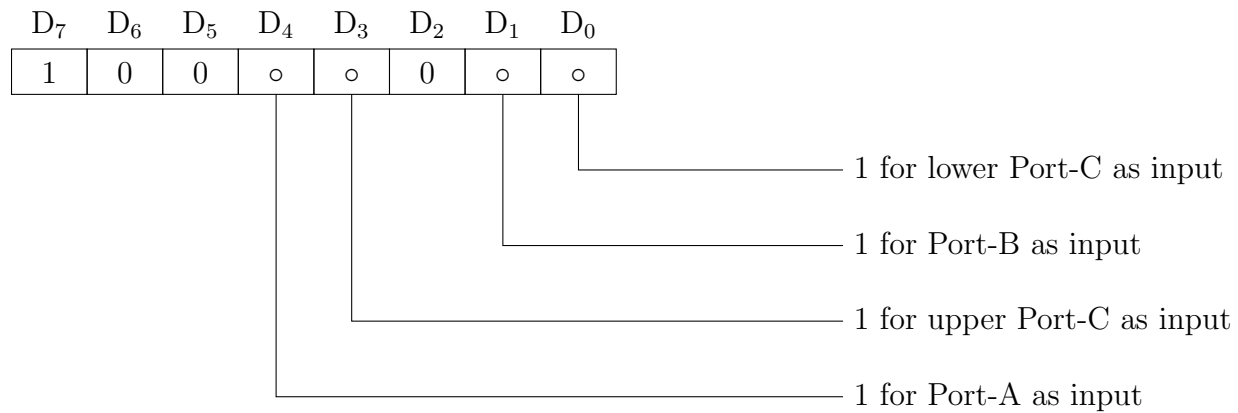

Logic controller

CW DB 82H ; Port-A output, Port-B input; MDE-0, I/O Mode.

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1	0	0	0	0	0	1	0

Seven Segment display

CW DB 80H ; Port-B output, Port-C output, Mode 0, I/O Mode

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1	0	0	0	0	0	0	0

Key Board interface

CW DB 90H ;Port-A input, Port-C output, Mode-0, I/O Mode


D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1	0	0	1	0	0	0	0

Elevator Interface

CW DB 80H ; Port-B output, Port-C output, Mode-0, I/O Mode

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
1	0	0	1	0	0	0	0

A.10 Flag register

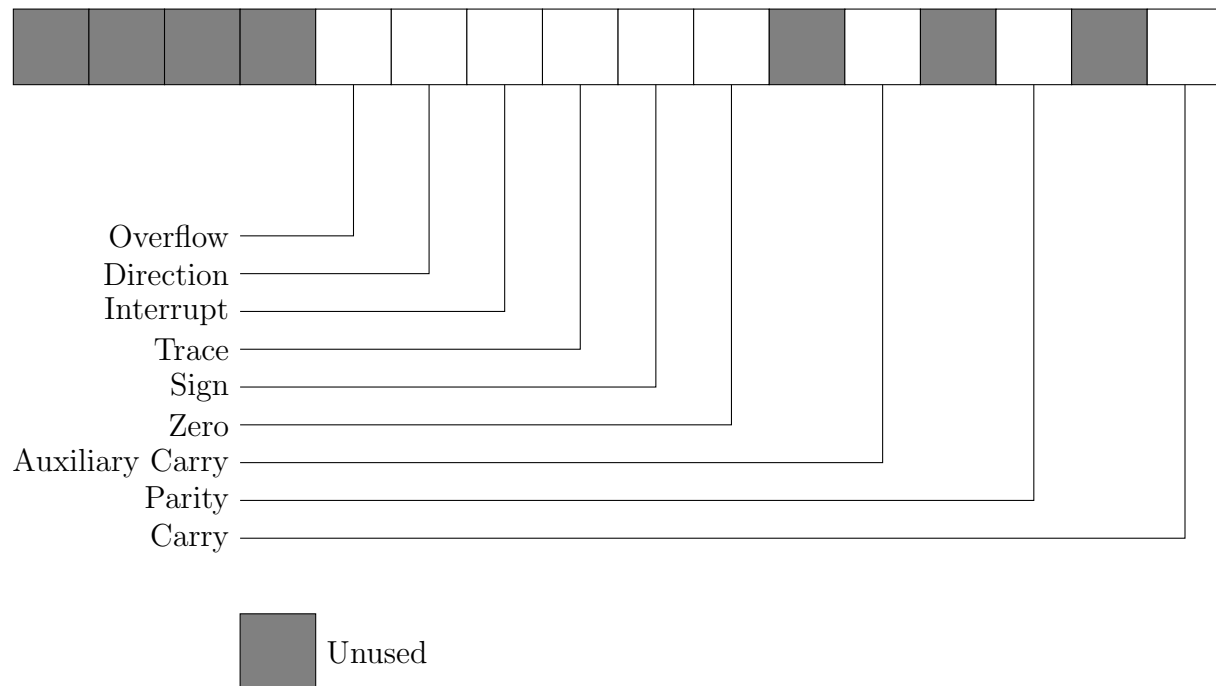

Flag	Function
CF-Carry Flag	=1 if high order bit carry/borrow =0 otherwise
PF-Parity Flag	=1 if low order 8-bit of result contain even parity =0 otherwise
AF-Auxiliary Flag	=1 if carry from/borrow to lower nibble of AL =0 otherwise
ZF-Zero Flag	=1 if result is zero =0 otherwise
SF-Sign Flag	=1 if MSB of result is 1 (−ve sign) =0 if MSB of result is 0 (+ve sign)
OF-Overflow Flag	=1 if result is out of range =0 otherwise